

Exercise 7: State Machine



Revision: October 10, 2013

1300 Henley Court | Pullman, WA 99163
(509) 334 6306 Voice and Fax



STUDENT		GRADER	
I am submitting my own work in this exercise, and I am aware of the penalties for cheating that will be assessed if I submit work for credit that is not my own.		#	Points Score
		1	14
		2	15
		3	15
		4	25
		5	25
		6	16
		T	110

Total Score

STUDENT		GRADER	
KEY.			
Print Name _____	WSU ID _____		
Sign Name _____	Date _____		

Estimated hours of work										
1	2	3	4	5	6	7	8	9	10	
1	2	3	4	5	6	7	8	9	10	
Weight										

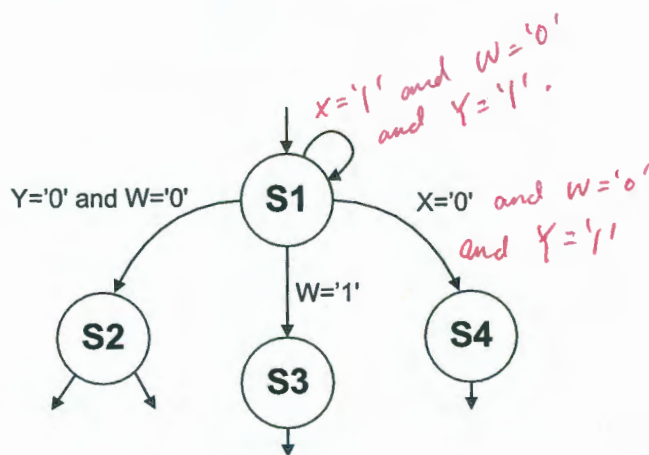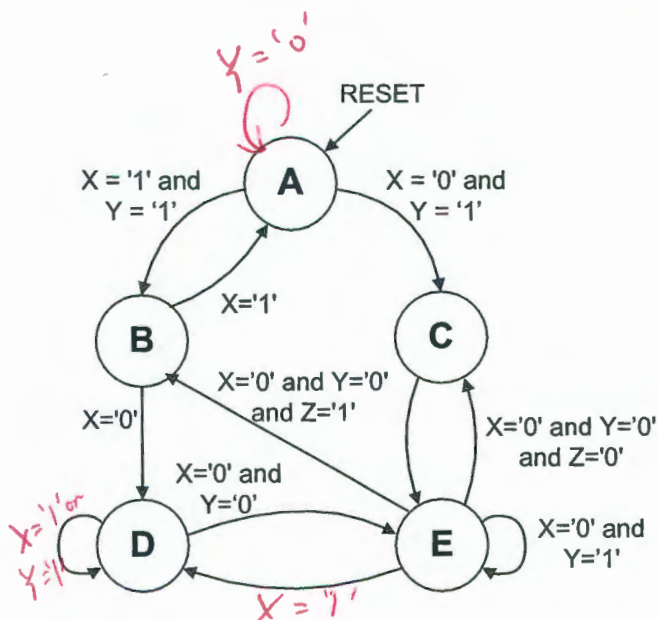
Problem 1. (10 points) Modify the state diagram branching conditions in the diagrams below as needed to ensure the sum and exclusion rules are obeyed in each case. You can add a holding conditions or change branch codes as desired.




Modify the S4 branch and holding condition only

Problem 2. (15 points) A vending machine should SELL an item if 30 cents is input. The machine has a coin sensor that can detect nickels, dimes, and quarters, and reject everything else. No change is given (i.e., if two quarters are input, simply assert SELL and keep the fifty cents). Sketch a state diagram to assert SELL when adequate coinage has been inserted.

N - nickel.
D - dime.
Q - quarter

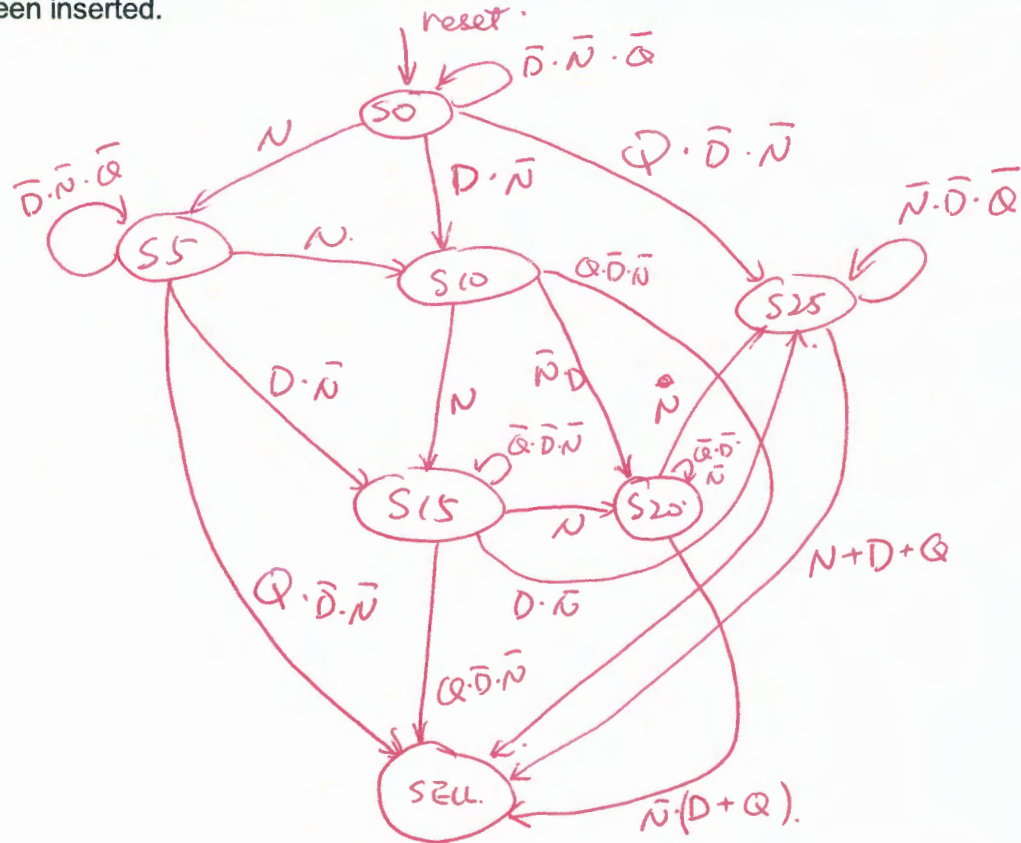


Problem 3. (15 points) Create a state diagram for a machine that can control a 4-button digital combination lock mechanism, unlocking only if the sequence B0-B3-B1 is detected.

 

Exercise 7: State Machine

 Problem 4. (25 points) Sketch a circuit for the state machines below.



	B _{PS}	
A _{PS}	0	1
0	1	φ
1	1	1

A_{NS}

	B _{PS}	
A _{PS}	0	1
0	0	φ
1	1	0

RED

	B _{PS}	
A _{PS}	0	1
0	X	φ
1	X	Y

B_{NS}

	B _{PS}	
A _{PS}	0	1
0	0	φ
1	0	1

GRN

Next-state maps


Output Maps

$$\Rightarrow A_{NS} = 1.$$

$$B_{NS} = \overline{B_{PS}} \cdot X + B_{PS} \cdot Y.$$

$$RED = A_{PS} \cdot \overline{B_{PS}}$$

$$GRN = B_{PS}.$$

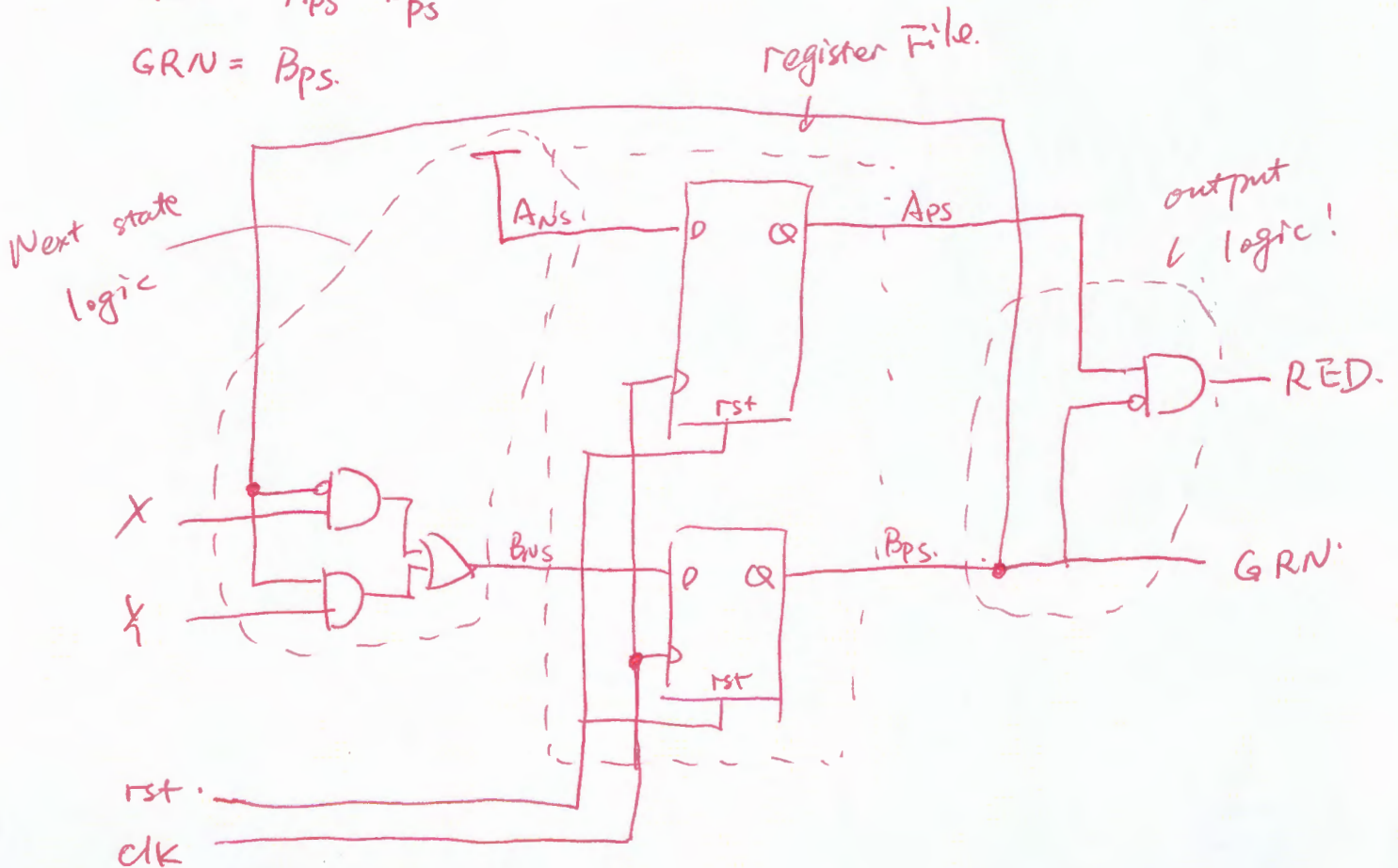

Exercise 7: State Machine

Problem 5. (25 points) Sketch a state diagram based on the following Verilog Code

```
module fsm (
    CLK, RST, X, Y, Z, RED, BLUE);
```

```
input CLK, RST, X, Y, Z;
output reg RED, BLUE;
```

```
localparam S1 = 2'd0;
localparam S2 = 2'd1;
localparam S3 = 2'd2;
localparam S4 = 2'd3;
```

```
reg [1:0] ps, ns;
```

```
always @ (ps, x, y, z)
begin
```

```
case (ps)
```

```
  S1: begin
```

```
    RED = 1'b0;
```

```
    BLUE = 1'b0;
```

```
    if (X == 1'b0) ns = S1;
```

```
    else ns = S2;
```

```
  end
```

```
  S2: begin
```

```
    RED = 1'b0;
```

```
    BLUE = 1'b1;
```

```
    if (X == 1'b0 && Y == 1'b0 && Z == 1'b0) ns = S2;
```

```
    else if (X == 1'b1 || Y == 1'b1) ns = S1;
```

```
    else if (Z == 1'b1 && X == 1'b0 && Y == 1'b0) ns = S3;
```

```
  end
```

```
  S3: begin
```

```
    RED = Y;
```

```
    BLUE = 1'b0;
```

```
    if (Y == 1'b1 && X == 1'b0 && Z == 1'b0) ns = S4;
```

```
    else if (X == 1'b0 && Y == 1'b0 && Z == 1'b0) ns = S3;
```

```
    else if (X == 1'b1 || Z == 1'b1) ns = S1;
```

```
  end
```

```
  S4: begin
```

```
    RED = 1'b1;
```

```
    BLUE = X;
```

```
    ns = S1;
```

```
  end
```

```
  default: begin
```

```
    RED = 1'b0;
```

```
    BLUE = 1'b0;
```

```
    ns = S1;
```

```
  end
```

```
endcase
```

```
end
```

```
always @ (CLK, RST)
```


```
begin
```

```
  if (RST == 1'b1) ps <= S1;
```

```
  else ps <= ns;
```

```
end
```

```
endmodule
```

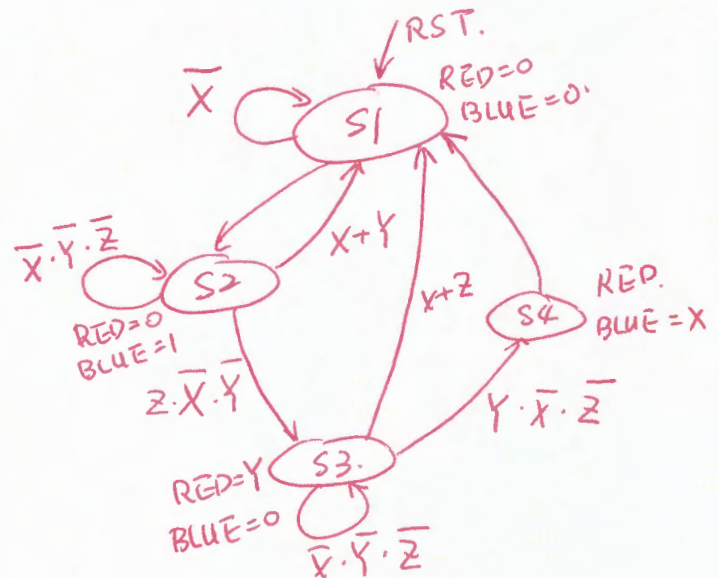


rst to state S1.


high active.

Exercise 7: State Machine

 
Problem 6. (16 points) Assign state codes to the state diagrams below, using unit-distance coding and/or matching state codes to outputs




*matching state
codes to outputs*

 

 *unit - distance
and matching state codes
to outputs.*



*matching state
codes to outputs*

 

*matching state codes
to outputs.*